

浙江大学 2024 年研究生入学考试

初试试题解析

试题代号: 840


试题名称: 电路原理

参考书: 电路—邱关源

试题及答案获取方式: 关注公粽号【梦马强哥电路课堂】，后台回复“24840”

一、【分析】考查电路方程。

电路如下图所示

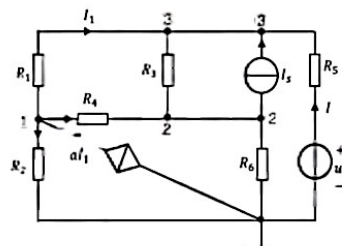

由题意易得

$$I = 0$$

节点电压方程如下

$$\begin{cases} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) u_{n1} - \frac{1}{R_4} u_{n2} - \frac{1}{R_3} u_{n3} = aI_1 \\ -\frac{1}{R_4} u_{n1} + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_6} \right) \frac{1}{R_4} u_{n2} - \frac{1}{R_3} u_{n3} = -I_s \\ u_{n3} = u_s \end{cases}$$

附加方程

$$I_1 = \frac{u_{n1} - u_{n3}}{R_1}$$

解得

$$\begin{cases} u_{n1} = \frac{60}{7} V \\ u_{n2} = \frac{24}{7} V \\ I_1 = -\frac{2}{7} A \end{cases}$$

对于①节点列KCL可得

$$\begin{cases} \frac{u_{n1}}{R_2} + \frac{u_{n1} - u_{n2}}{R_6} - \alpha I_1 = 0 \\ I_1 = -\frac{2}{7} A \end{cases}$$

得


$$\alpha = -\frac{9}{2} A$$

$$P_{I_s} = (u_{n1} - u_{n2}) I_s = \frac{60}{7} \times 1 = \frac{60}{7} W$$


I_s 发出 $\frac{60}{7} W$ 功率。

二、【分析】考查戴维南定理。

(1)当开关 k_1 打开时,求cd左侧戴维南等效电路如下图所示

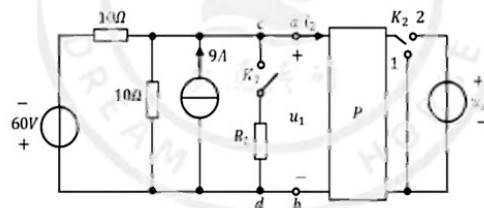

求 U_{OC1} 电路如下图所示

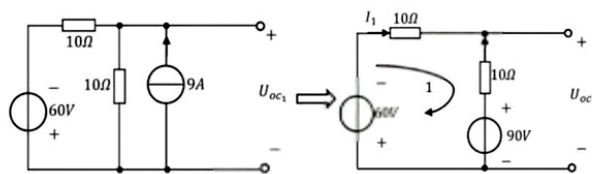

对回路1列KVL可得

$$(10 + 10)I_1 + 90 + 60 = 0$$

解得


$$I_1 = -7.5 A$$

B站up: 犹如雨下
则

公众号: 梦马强哥电路课堂

$$U_{OC1} = 10I_1 + 90V = 15V$$

求 R_{eq1} 电路如下图所示

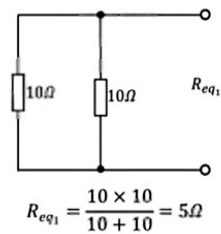


求 ab 右侧戴维南等效电路。

设

$$u_1 = R_{eq2}i_2 + ku_s$$

则整体电路等效如下图所示

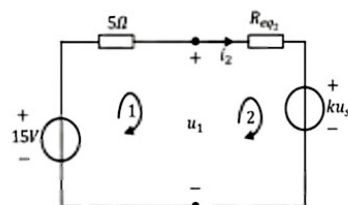

当 $u_s = 0$ 时, $u_1 = 10V$, 则

$$\frac{R_{eq2}}{5 + R_{eq2}} \times 15 = 10$$

解得

$$R_{eq2} = 10\Omega$$

当 $u_s = 60V$ 时, $u_1 = 18V$ 。

对回路 1 列KVL可得

$$5i_2 + u_1 - 15 = 0$$

解得

$$i_2 = -0.6A$$

对回路 2 列KVL可得

$$i_2 R_{eq2} + 60k - u_1 = 0$$

B站up: 犹如雨下
 带入整理可得


公众号: 梦马强哥电路课堂

$$-6 + 60k - 18 = 0$$


解得

$$k = 0.4$$

故当 $u_s = 100V$ 时, ab 右端戴维南等效电路如下图所示

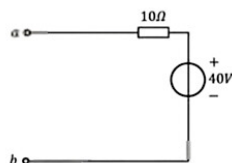


(2) 当 $u_s = 100V$, 开关 k_2 闭合时电路如下图所示

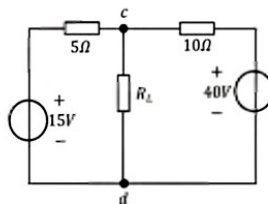

以 R_L 为感兴趣支路求戴维南电路。

求 U_{OC3} 电路如下图所示

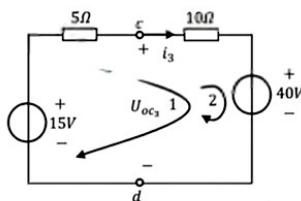

对回路 1 列KVL可得

$$(10 + 5)i_3 + 40 - 15 = 0$$

解得

$$i_3 = -\frac{5}{3}A$$

对回路 2 列KVL可得

$$10i_3 + 40 - U_{OC3} = 0$$

B站up: 犹如雨下
解得


公众号: 梦马强哥电路课堂

$$U_{OC3} = \frac{70}{3} V$$

R_{eq3} 易得

$$R_{eq3} = 5 // 10 = \frac{10}{3} \Omega$$

故戴维南电路如下图所示

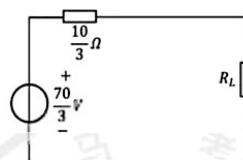

故当 $R_L = \frac{10}{3} \Omega$ 时, R_2 取得最大功率

$$R_{Lmax} = \frac{U_{OC}^2}{4R_L} = \frac{245}{6} W$$

三、【分析】考查矩阵方程。

(1) 3、5、6 为树支, 则 1、2、4、7 为连支

$$B_f = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 4 \\ 7 \end{matrix} & \begin{bmatrix} 1 & 0 & -1 & 0 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 & -1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & -1 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 1 \end{bmatrix} \end{matrix}$$

(2)

$$Z = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} R_1 & & & & & & \\ & \frac{1}{j\omega C_2} & & & & \frac{j}{j\omega C_3} & \\ & & j\omega L_3 & j\omega M & & & \\ & & j\omega M & j\omega L_4 + R_4 & & & \\ & & & & R_5 & & \\ & & & & & \frac{1}{j\omega C_6} & \\ & & & & & & R_7 \end{bmatrix} \end{matrix}$$

(3)

$$\dot{U}_s = [\dot{U}_{s1} \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad U_{sT}]^T$$

(4)

$$\boldsymbol{l}_s = [0 \ 0 \ 0 \ 0 \ I_{s5} \ 0 \ 0]^T$$

(5)


$$\boldsymbol{Z}_1 = \boldsymbol{B}_f \cdot \boldsymbol{Z} \cdot \boldsymbol{B}_f^T$$

(6)

$$\boldsymbol{B}_f \cdot \boldsymbol{Z} \cdot \boldsymbol{B}_f^T \cdot \boldsymbol{l}_6 = -\boldsymbol{B}_f \cdot \boldsymbol{Z} \cdot \boldsymbol{l}_s - \boldsymbol{B}_f \dot{\boldsymbol{U}}_s$$

四、【分析】考查二端口网络与复频域分析

(1) 电路如下图所示

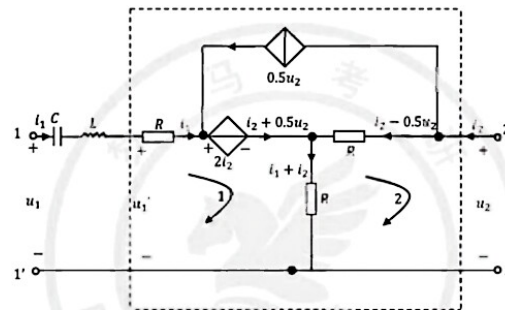

对回路 1 列KVL可得

$$2i_1 + 2i_2 + 2(i_1 + i_2) - u_1' = 0$$

对回路 2 列KVL可得


$$-2(i_2 - 0.5u_2) + u_2 - 2(i_1 + i_2) = 0$$

解得

$$\begin{cases} u_1' = 4i_1 + 4i_2 \\ u_2 = i_1 + 2i_2 \end{cases}$$

$$\boldsymbol{Z} = \begin{bmatrix} 4 & 4 \\ 1 & 2 \end{bmatrix}$$

(2) 运算电路如下图所示

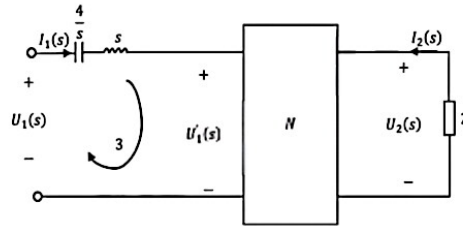

由Z参数得

$$\begin{aligned} U_1'(s) &= 4I_1(s) + 4I_2(s) = 4I_1(s) + 4 \times \frac{-U_2(s)}{2} \\ U_2(s) &= I_1(s) + 2I_2(s) = I_1(s) + 2 \times \frac{-U_2(s)}{2} \end{aligned}$$

解得

$$\begin{cases} U_1'(s) = 4I_1(s) - 2U_2(s) \\ U_2(s) = I_1(s) - U_2(s) \end{cases}$$

对回路3列KVL可得

$$U_1(s) = \left(s + \frac{4}{s}\right)I_1(s) + U_1'(s) = \left(s + \frac{4}{s}\right)I_1(s) + 3I_1(s) = \left(s + \frac{4}{s} + 3\right)I_1(s)$$

故

$$H(s) = \frac{U_2'(s)}{U_1(s)} = \frac{\frac{1}{2}I_1(s)}{\left(s + \frac{4}{s} + 3\right)I_1(s)} = \frac{\frac{1}{2}s}{s^2 + 3s + 4}$$

(3) 零点: 当 $\frac{1}{2}s = 0 \Rightarrow s = 0$ 为零点

极点: 当 $s^2 + 3s + 4 = 0 \Rightarrow p_1 = -\frac{3}{2} + j\frac{\sqrt{7}}{2}$, $p_2 = -\frac{3}{2} - j\frac{\sqrt{7}}{2}$ 为极点。

五、【分析】考查均匀传输线

方法: 从右向左求始端, 从左向右求终端。

(1)

$$\gamma_1 = \alpha + j\beta = \sqrt{2} \times 10^{-3} \angle 45^\circ = 10^{-3} + j10^{-3}$$

$$\begin{cases} \lambda = v \cdot T = \frac{v}{f} \Rightarrow \lambda = \frac{2\pi}{\beta} \\ v = \frac{\omega}{\beta} \end{cases}$$

$$U(x) = U_2 \cos \beta x + jZ_C I_2 \sin \beta x$$

$$I(x) = I_2 \cos \beta x + jZ_C \frac{\dot{U}_2}{Z_C} \sin \beta x$$

$$Z_{C3} = \frac{U(x)I_2 = 0}{I(x)} = \frac{\dot{U}_2 \cos \beta x}{j \frac{\dot{U}_2}{Z_C} \sin \beta x} = -jZ_C \cdot \frac{1}{\tan \beta x} = -j100\sqrt{3} \cdot \frac{1}{\tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{6}} = -j100\Omega$$

$$\xrightarrow{\text{分子分母同乘 } 1 - \cos \beta x} \frac{Z_2 + jZ_C \tan \beta x}{1 + j \frac{Z_2}{Z_C} \tan \beta x}$$

$$= \frac{100 + j50 + j50\sqrt{2} \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}}{1 + j \frac{100 + j50}{50\sqrt{2}} \cdot \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}} = \frac{(50\sqrt{2})^2}{100 + j50} = 40 - j20$$

$$Z_{bb'} = Z_{C2} // Z_{C1} = (-j100) // (40 - j20) = 25 - j25\Omega$$

(2) 因为 $Z_{bb'} = Z_{C1}$ 发生阻抗匹配, 则

$$\dot{U}_s = 25 \angle 30^\circ$$

$$I = \frac{\dot{U}_s}{Z_1 + Z_{C1}} = \frac{25 \angle 30^\circ}{25 + 25 - j25} = \frac{\sqrt{5}}{5} \angle 56.57^\circ A$$


$$i(t) = \frac{\sqrt{10}}{5} \sin(\omega t + 56.57^\circ) A$$

六、【分析】考查非正弦周期信号与二端口网络结合

(1) 根据二端口回转器特性, 电路右侧为电容


$$\frac{\dot{U}_3}{I_3} = \frac{-3I_4}{\frac{1}{3}\dot{U}_4} \xrightarrow{I_4 \text{ 与 } I_3 \text{ 关联}} 9 \frac{1}{j\omega L_2} = -j \frac{9}{\omega L_2}$$

电路等效如下图所示

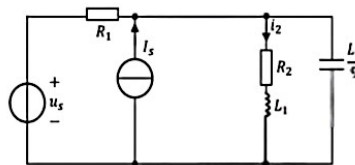

$$P = I_1^2 R_1 + I_2^2 R_2 \Rightarrow 175 = 25 \times 4 + 25 R_2 \Rightarrow R_2 = 3\Omega$$

(2) 当直流源单独作用时, 电路如下图所示

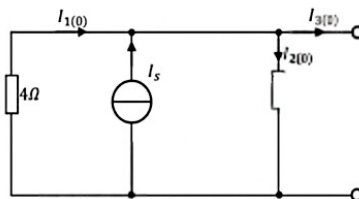


经分流公式得

$$I_{1(0)} = 3A; I_{2(0)} = 4A; I_{3(0)} = 0A$$

故

$$I_{1(1)} = \sqrt{I_1^2 - I_{1(0)}^2} = 4A; I_{2(1)} = \sqrt{I_2^2 - I_{2(0)}^2} = 3A; I_{3(1)} = \sqrt{I_3^2 - I_{3(0)}^2} = 5A$$


当交流单独作用时, 电路如下图所示

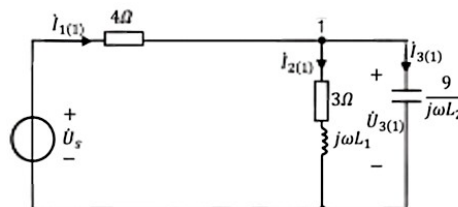

设 $\dot{U}_{3(1)} = \dot{U}_3 \angle 0^\circ$, 对 1 节点列 KCL 可得

$$\dot{I}_{1(1)} = \dot{I}_{2(1)} + \dot{I}_{3(1)}$$

相量图如下图所示

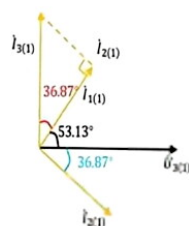

根据几何分析得

$$\dot{I}_{1(1)} = 4 \angle 53.13^\circ; \dot{I}_{2(1)} = 3 \angle -36.87^\circ; \dot{I}_{3(1)} = 5 \angle 90^\circ$$

则

B站up: 犹如雨下

公众号: 梦马强哥电路课堂

$$\tan(0^\circ - (-36.87^\circ)) = \frac{\omega L_1}{3} = \frac{3}{4} \Rightarrow \omega L_1 = \frac{9}{4} \Omega \Rightarrow L_1 = \frac{9}{4} \text{mH}$$

$$\dot{U}_{3(1)} = (R_2 + j\omega L_1) i_{2(1)} = \frac{45}{4} \angle 0^\circ$$

则

$$\frac{\dot{U}_{3(1)}}{i_{3(1)}} = \frac{9}{\omega L_2} \Rightarrow L_2 = 4 \text{mH}$$


(3) 对回路列KVL易得

$$\dot{U}_s = R_1 i_{1(1)} + \dot{U}_{3(1)} = 4 \times 4 \angle 53.13^\circ + \frac{45}{4} \angle 0^\circ = 24.47 \angle 31.55^\circ \text{V}$$

$$U_s = 24.47 \text{V}$$

七、【分析】考查非正弦周期信号是二端口网络+振幅


(1) 当 $U_s = 50\text{V}$ 单独作用时, 电路如下图所示

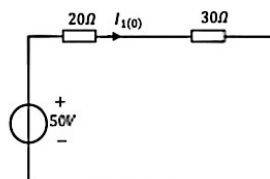

$$I_{1(0)} = \frac{50}{20 + 30} = 1 \text{A}$$

$$P_a = I_{1(0)}^2 \times R_2 = 30 \text{W}$$

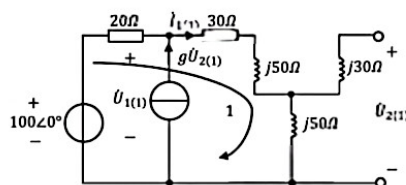当 $\dot{U}_s = 100 \angle 0^\circ \text{V}$ 时, 电路如下图所示



对回路 1 列KVL可得

$$20(i_{1(1)} - g\dot{U}_{2(1)}) + (30 + j100)i_{1(1)} - 100 \angle 0^\circ = 0$$

$$\dot{U}_{2(1)} = i_{1(1)} \cdot j50$$

解得

$$i_{1(1)} = 2 \angle 0^\circ$$

$$P_{(1)} = I_{1(1)}^2 R_2 = 120W$$

则


$$P = P_{(0)} + P_{(1)} = 150W$$

(2) 回转器方程

$$\begin{cases} \dot{U}_2 = -r \cdot \dot{I}_3 \\ \dot{U}_3 = r \cdot \dot{I}_2 \end{cases}$$

$$\frac{\dot{U}_{2(1)}}{\dot{I}_{3(1)}} = \frac{-r \dot{I}_{3(1)}}{\frac{\dot{U}_{3(1)}}{r}} = -r^2 \frac{\dot{I}_{3(1)}}{\dot{U}_{3(1)}} = -r^2 \frac{1}{j\omega L_3} = -j \frac{r^2}{30} \Omega$$

电路等效如下图所示

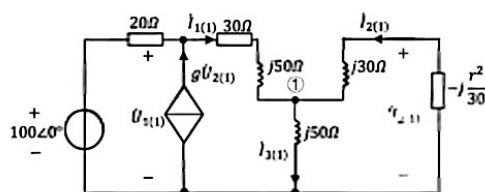

对 1 节点列 KCL 可得

$$I_{1(1)} + I_{2(1)} = I_{3(1)}$$


若要使 $I_{1(1)} = I_{2(1)}$, 则必有

$$I_{3(1)} = 0$$

故电路最右侧发生串联谐振, 则

$$j \left(30 - \frac{r^2}{30} \right) = 0 \Rightarrow r = 30 \Omega$$

电路再次等效如下图所示

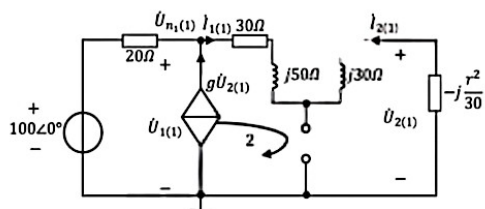

列写节点电压方程

$$\begin{cases} \left(\frac{1}{20} + \frac{1}{30 + j50}\right) \dot{U}_{n1(1)} = \frac{100\angle 0^\circ}{20} + 0.1\dot{U}_{2(1)} \\ \dot{U}_{2(1)} = \frac{\dot{U}_{n1(1)}}{30 + j50} \times (-j30) \end{cases}$$

解得

$$\dot{U}_{n1} = 48.26\angle -6.52^\circ V; \quad \dot{U}_{2(1)} = 24.83\angle -155.56^\circ V$$

则

$$u_2(t) = 24.83\sqrt{2} \sin(\omega t - 155.56^\circ) V$$

$$P_{R_2} = 30 + \left(\frac{U_{n1}}{\sqrt{30^2 + 50^2}}\right)^2 \times 30 = 50.55 W$$

(3) 设 $\dot{I}_1 \angle 0^\circ$, 则

$$\dot{U}_{2(1)} = -j30 \cdot \dot{I}_{1(1)} \angle 0^\circ = 30\dot{I}_{1(1)} \angle -90^\circ = U_{2(1)} \angle -90^\circ$$

那么

$$g \cdot \dot{U}_{2(1)} = g U_{2(1)} \angle -90^\circ$$

$$\frac{g \cdot \dot{U}_{2(1)}}{\dot{U}_1 \angle \varphi_{u_1}} = \frac{g U_2}{U_1} \angle -135^\circ$$

则

$$\varphi_{u_1} = 45^\circ$$

对回路 2 列 KVL 可得

$$\dot{I}_{1(1)}(R_2 + j50) = U_1 \angle 45^\circ$$


$$\dot{I}_1 (R + j50) = U_1 \angle 45^\circ$$

故


$$R = 50 \Omega$$

八、【分析】

(1)

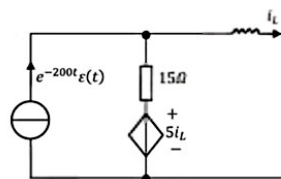

作运算电路图如下图所示:

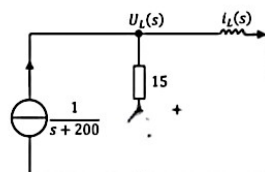

列节点电压方程可得:

$$\begin{cases} \left(\frac{1}{15} + \frac{1}{0.1s}\right) U_L(s) = \frac{1}{s+200} + \frac{1}{3} I_L(s) \\ U_L(s) = 0.1s \cdot I_L(s) \end{cases}$$

整理可得

$$I_L(s) = \frac{150}{(s+100)(s+200)} = \frac{1.5}{s+100} + \frac{-1.5}{s+200}$$

则

$$i_L(t) = (1.5e^{-100t} - 1.5e^{-200t})\varepsilon(t)A$$


(2) 当 K_1 闭合时

$$\tau = \frac{1}{100} = \frac{0.1}{R_{eq}}$$


解得

$$R_{eq} = 10\Omega$$

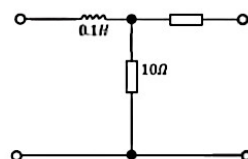要使 K_1 闭合时 $i_L(t)$ 为 K_1 打开时的 2 倍, 则 K_1 打开后, 电路时间常数不变, $i_L(\infty)$ 为原来的一半, 故可将 P 等效为如下图所示




当 K_1 闭合时电路达到稳态, 如下图所示

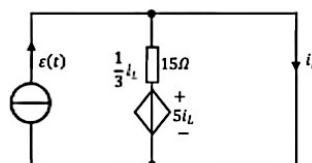


$$i_L = \frac{1}{3}i_L + 1$$

$$i_L(0_-) = 1.5A$$


对L左侧进行戴维南等效, 如下图所示

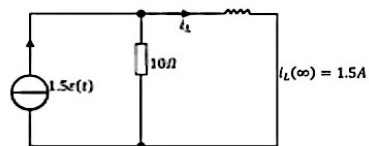

当 K_1 打开时, 电路图如下图所示:

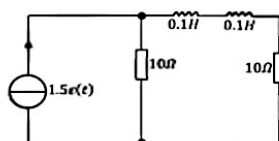

作运算电路模型如下图所示

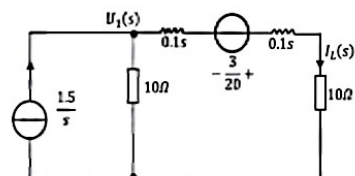

列节点电压方程可得


$$\left(\frac{1}{10} + \frac{1}{10 + 0.2s}\right)U_1(s) = \frac{1.5}{s} - \frac{\frac{3}{20}}{10 + 0.2s}$$

$$U_1(s) = \frac{7.5s + 750}{s(s + 100)}$$


$$i_L(s) = \frac{1.5}{s} - \frac{1}{10}U_1(s) = \frac{1.5}{s} - \frac{0.75s + 75}{s(s + 100)} = \frac{1.5}{s} - \frac{0.75}{s} = \frac{0.75}{s}$$

所以 $i_L(t) = \frac{3}{4}\varepsilon(t)A$, 无过渡过程。

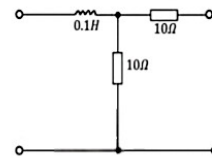
(3)要使 $i_L(t) = 2i_2(t)$, 故可将P进一步等效为如下图所示




对NIC及其右侧电路进行等效如下图所示

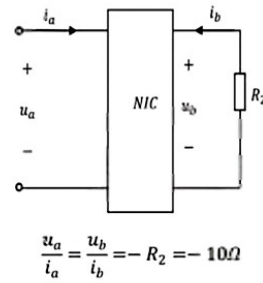

原电路可等效如下图所示

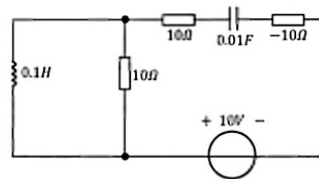

作运算电路模型如下图所示

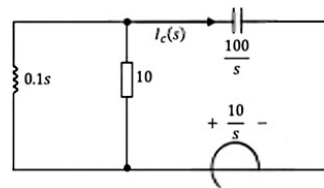

$$I_C(s) = \frac{\frac{10}{s}}{0.1s//10 + \frac{100}{s}} = \frac{s+100}{s^2+10s+1000}$$

$$\Delta = 10^2 - 4 \times 1000 = -3900 < 0$$

所以电容电流震荡。